

Problem Set #8 The symmetrical components of unsymmetrical phasors

8-1 (Keyhani Lecture)

Given


$$Z_{abc} = \begin{bmatrix} Z & 0 & 0 \\ 0 & Z & 0 \\ 0 & 0 & Z \end{bmatrix}$$

Find Z_{012} .

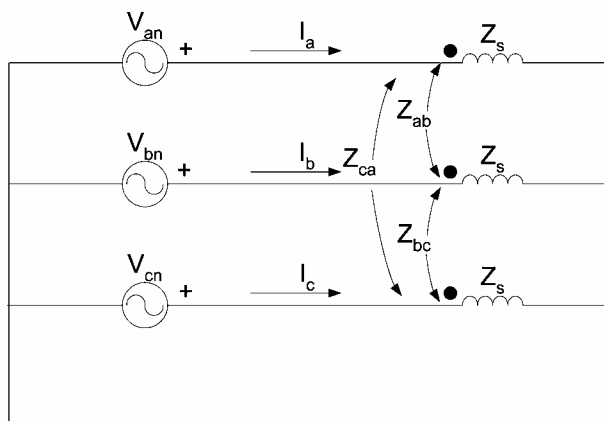8-2 (Keyhani Lecture)

Consider the circuit shown below. Suppose $V_{an}=100\angle 0^\circ$, $V_{bn}=50\angle 180^\circ$, $V_{cn}=50\angle 180^\circ$, $Z_s=8+j10$, and $Z_{ab}=Z_{bc}=Z_{ca}=j4$.

- Calculate I_a , I_b , and I_c without using symmetrical components.
- Calculate I_a , I_b , and I_c using symmetrical components.



8-3 (Keyhani Lecture)


Frequently, T is defined as

$$\frac{1}{\sqrt{3}} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

When this is the case, T is unitary.


- Prove it. A matrix is unitary when its inverse equals its transpose conjugate.
- Defining T as in part a), prove that $S_{3\phi} = V_{abc}^T I_{abc}^* = V_{012}^T I_{012}^*$. This result is called the invariance of power condition and makes a strong case for the corresponding definition of T.

8-4 (Keyhani Lecture)
Three-phase system

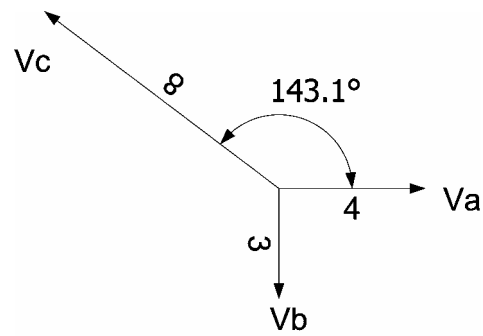


feeding a three-phase balanced load as shown:


a)

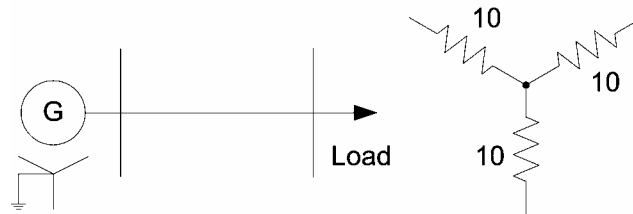

b)

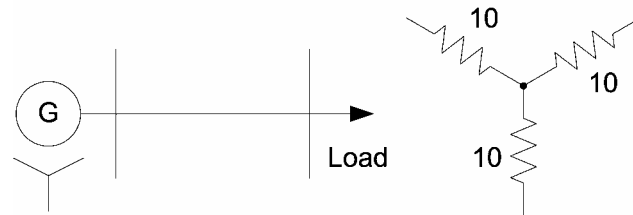

c)

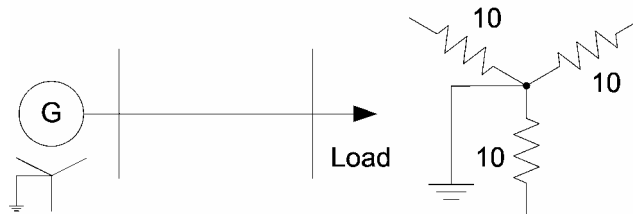

Compute I_0 , I_1 , I_2 , and I_a for part a, b, and c.