

## Problem Set #1 Basic concepts – complex algebra and three-phase balanced circuits

**1-1** (Grainger and Stevenson, Jr. Chapter 1, Prob 1.12)

Evaluate the following expressions in polar form:


Solution:

- a)  $a-1 = 1.732\angle 150^\circ$
- b)  $1-a^2+a = 2.00\angle 60^\circ$
- c)  $a^2+a+j = 1.414\angle 135^\circ$
- d)  $ja+a^2 = 1.932\angle 225^\circ$

**1-2** (Grainger and Stevenson, Jr. Chapter 1, Prob 1.13)

Three identical impedances of  $10\angle -15^\circ \Omega$  are Y-connected to balanced three-phase line voltages of 208 V. Specify all the line and phase voltages and the currents as phasors in polar form with  $V_{ca}$  as reference for a phase sequence of  $abc$ .

Solution:

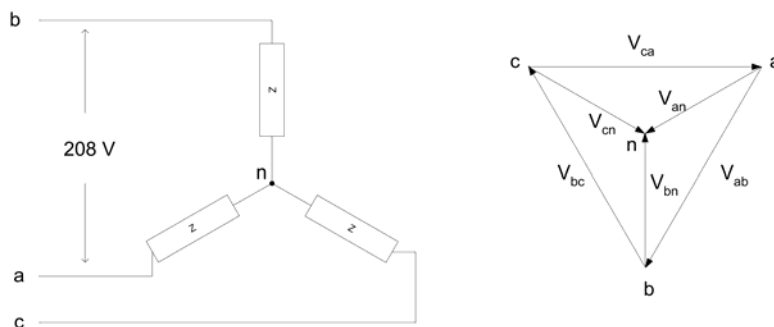

Since  $V_{ca}=208\angle 0^\circ$  V,  $V_{an}=120\angle 210^\circ$  V,  $V_{bn}=120\angle 90^\circ$  V,  $V_{cn}=120\angle -30^\circ$  V. Therefore,


$$I_a = \frac{V_{an}}{Z} = 12\angle 225^\circ \text{ A}, \quad I_b = \frac{V_{bn}}{Z} = 12\angle 105^\circ \text{ A}, \quad I_c = \frac{V_{cn}}{Z} = 12\angle -15^\circ \text{ A}$$

**1-3** (Grainger and Stevenson, Jr. Chapter 1, Prob 1.14)

In a balanced three-phase system the Y-connected impedances are  $10\angle 30^\circ \Omega$ . If  $V_{bc}=416\angle 90^\circ$  V, specify  $I_{cn}$  in polar form.

Solution:
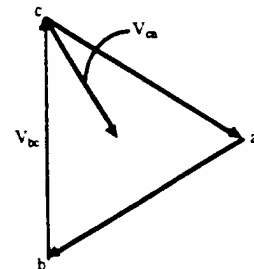
$$\begin{aligned} \frac{416}{\sqrt{3}} &= 240 \text{ V} \\ V_{cn} &= 240\angle -60^\circ \text{ V} \\ I_{cn} &= \frac{240\angle -60^\circ}{10\angle 30^\circ} = 24\angle -90^\circ \text{ A} \end{aligned}$$



**1-4** (Grainger and Stevenson, Jr. Chapter 1, Prob 1.16)

Determine the current drawn from a three-phase 440-V line by a three-phase 15-hp motor operating at full load, 90% efficiency, and 80% power-factor lagging. Find the values of P and Q drawn from the line.

**Solution:**

$$\begin{aligned} |I| &= \frac{15 \times 746}{\sqrt{3} \times 440 \times 0.9 \times 0.8} = 20.39 \text{ A} \\ P &= \sqrt{3} \times 440 \times 20.39 \times 0.8 = 12,431 \text{ W drawn from line} \\ Q &= \sqrt{3} \times 440 \times 20.39 \times 0.6 = 9,324 \text{ var drawn from line} \end{aligned}$$

**1-5** (Grainger and Stevenson, Jr. Chapter 1, Prob 1.17)

If the impedance of each of the three lines connecting the motor of Problem 4 (or Prob 1.16) to a bus is  $0.3+j1.0 \Omega$ , find the line-to-line voltage at the bus which supplies 440V at the motor.

**Solution:**

$$I = 20.39(0.8 - j0.6) = 16.31 - j12.23 \text{ A}$$

When the reference is voltage to neutral of the motor at the terminal where  $I$  is calculated, or  $440/\sqrt{3} = 254 \angle 0^\circ$  V, the supply bus voltage to neutral is

$$\begin{aligned} 254 + j0 + (0.3 + j1.0)(16.31 - j12.23) &= 271.1 + j12.64 \\ \text{Line-to-line voltage } |V| &= \sqrt{3} |271.1 + j12.64| = 470 \text{ V} \end{aligned}$$

**1-6** (Grainger and Stevenson, Jr. Chapter 1, Prob 1.24)

Draw the single-phase equivalent circuit for the motor (an emf in series with inductive reactance labeled  $Z_m$ ) and its connection to the voltage supply described in Problem 4 and 5 (or Prob. 1.16 and 1.17). Show on the diagram the per-unit values of the line impedance and the voltage at the motor terminals on a base of 20 kVA, 440V. Then using per-unit values, find the supply voltage in per unit and convert the per-unit value of the supply voltage to volts.

Solution:

Per-unit base calculations:

$$\text{Base } Z = \frac{(0.44)^2 \times 1000}{20} = 9.68 \text{ per unit}$$

$$R = \frac{0.3}{9.68} = 0.031 \text{ per unit}$$

$$X = \frac{1.0}{9.68} = 0.1033 \text{ per unit}$$

$$\text{Base } I = \frac{20,000}{\sqrt{3} \times 440} = 26.24 \text{ A}$$

$$I = \frac{20.39}{26.24} = 0.777 \text{ per unit}$$

Voltage calculations:

$$V = 1.0 + 0.777 (0.8 - j0.6) (0.031 + j0.1033)$$


$$= 1.0 + 0.777 \times 0.1079 \angle 36.43^\circ$$

$$= 1.0 + 0.0674 + j0.0498 = 1.0686 \angle 2.97^\circ \text{ per unit}$$

$$|V_{LL}| = 1.0686 \times 440 = 470 \text{ V}$$
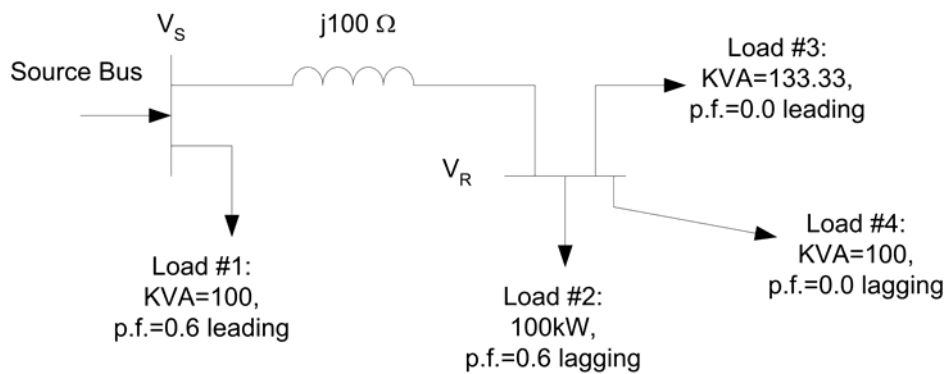
### 1-7 (Keyhani Lecture 1)

Consider a 3- $\phi$  distribution feeder as shown below:



Computer the following:

- 1) The source voltage  $V_S$ , if  $V_R$  is to be maintained at 4.4 kV ( $V_R=4.4$  kV line value).
- 2) The source current and power supplied by the source.
- 3) The total complex power supplied by the source.
- 4) How much reactive power should be connected to the source bus for obtaining unity power factor at the source bus?

Solution:

Load #1:

p.f.=0.6, leading,  $\cos\theta=0.6$ ,  $\sin\theta=-0.8$ ,

$$S_1=100\times 0.6\text{kW}-j100\times 0.8\text{kVar}=60\text{kW}-j80\text{kVar};$$

Load#2:

p.f.=0.6, lagging,  $\cos\theta=0.6$ ,  $\sin\theta=0.8$ ,

$$S_2=100\text{kW}+j100\times 0.8/0.6\text{kVar}=100\text{kW}+j133.33\text{kVar};$$

Load#3:

p.f.=0.0, leading,  $\cos\theta=0.0$ ,  $\sin\theta=-1.0$ ,

$$S_3=-j133.33\text{kVar};$$

Load#4:

p.f.=0.0, lagging,  $\cos\theta=0.0$ ,  $\sin\theta=1.0$ ,

$$S_4=j100\text{kVar};$$

$$1) S_R=S_2+S_3+S_4=100\text{kW}+j100\text{kVar}$$

Assuming  $V_{R,L-n}$  has a phase angle of  $0^\circ$ ,

$$S_R = 3V_{R,L-n}I_{LR}^*, \quad I_{LR} = \left( \frac{100 + j100}{3 \cdot \frac{4.4}{\sqrt{3}} \angle 0^\circ} \right)^* = 13.14 - j13.14 \text{ A}$$

$$V_{s,L-n} = V_{R,L-n} + I_{LR}Z_L = \frac{4400}{\sqrt{3}} \angle 0^\circ + (13.14 - j13.14) \times j100 \text{ V} = 4.02 \angle 16.35^\circ \text{ kV}$$

$$|V_{s,L-L}| = \sqrt{3} \cdot 4.02 \text{ kV} = 6.95 \text{ kV}$$

$$2) I_{L1} = \left( \frac{60 - j80}{3 \cdot 4.02 \angle 16.35^\circ} \right)^* = 2.91 + j7.77 \text{ A} = 8.29 \angle 69.48^\circ \text{ A}$$

$$I_s = I_{L1} + I_{LR} = 16.92 \angle -18.5^\circ \text{ A}$$

$$\theta = \angle V_{s,L-n} - \angle I_s = 16.35^\circ - (-18.5^\circ) = 34.85^\circ, \quad \text{pf} = \cos\theta = 0.82$$

$$3) S_s = 3V_{s,L-n}I_s^* = 3 \times 4.02 \angle 16.35^\circ \times 16.92 \angle 18.5^\circ \text{ kVA} \\ = 204.06 \angle 34.85^\circ \text{ kVA} = 167.46 \text{ kW} + j116.61 \text{ kVar}$$

$$4) S_c = -j116.61 \text{ kVar}$$