

ECE 301 Comprehensive Notes

Christopher J. Atherton

April 6, 2009

1 Dynamic Programming (Lecture 1)

With dynamic programming, you can figure out how to meet deadlines. This is required study for those unable to make it to class before 8:30.

2 Basic Linear Circuit Analysis Review (Lectures 1–2)

2.1 Linear Resistive Circuits

A few important facts (you already know).

- If the circuit is linear and ideal, then $V_n = R_n I_n$ (Ohm's Law).
- There are two kinds of sources.
 - Voltage source - always maintains a certain voltage across its terminals.
 - Current source - always maintains a certain current across its terminals.
- Solving the circuit requires $2n$ equations for n nodes.

– n from Ohm's Law.

$$\begin{cases} V_1 - R_1 I_1 = 0 \\ \vdots \\ V_n - R_n I_n = 0 \end{cases}$$

– n from KCL and KVL.

$$\begin{cases} \sum i = 0 \\ \sum v = 0 \end{cases}$$

- When there are many sources, superposition is applied.

2.2 Other Circuit Elements

The capacitor and inductor, obviously.

- Capacitor (Relation: $i = C dv/dt$)
- Inductor (Relation: $v = L di/dt$)

And these things cause there to be differential equations when solving the circuit.

2.3 Transients and Response

The inst. ran thru this in a very convoluted manner. Know that *transients* are changes in state (requires some form of memory). They arise from *initial state* and *inputs*.

- Steady-state (or forced, or particular) response
- Zero-input response
- Zero-state response - from input

And here's some other random terms.

- Stable - A system where there may be transients that die out
- Unstable - A system where there are transients that don't die out

At the end of the lecture, he dumped a bunch of random terms on us in rapid fire mode.

- Initial response
- Inputs response
- Total response
- Forced response
- Zero-input response
- Zero-state response
- Total transients

I might fix this later. Whatever Y(V_V)Y ...

2.4 Analysis

Suppose you have a circuit containing a 12 V source, a $R \Omega$ resistor, a L H inductor, and a C F capacitor in series, and that the circuit has been on for a long time. Then clearly for all time t , the voltage across the capacitor, y , is 12 as the transient term has died.

Now suppose that the KVL equation for this circuit is given by $y'' + 5y' + 6y = 12$, where y is the voltage across the capacitor.

$$y(t) = A$$

$$y'(t) = 0$$

$$y''(t) = 0$$

$$6(A) = 12$$

$$y(t) = A = 2$$

Again, because the transient term has died (the circuit having been on for a long time), y is given by the particular solution to the differential equation alone, which is 2.

Now suppose the equation is changed to $y'' + 5y' + 6y = e^{-t}$.

$$y(t) = Ae^{-t}$$

$$y'(t) = -Ae^{-t}$$

$$y''(t) = Ae^{-t}$$

$$Ae^{-t} - 5Ae^{-t} + 6Ae^{-t} = e^{-t}$$

$$7A = 1$$

$$A = \frac{1}{7}$$

$$y(t) = \frac{1}{7}e^{-t}$$

This time the equation is $y'' + 5y' + 6y = e^{2t}$.

$$y(t) = Ae^{2t}$$

$$y'(t) = 2Ae^{2t}$$

$$y''(t) = 4Ae^{2t}$$

$$4Ae^{2t} + 10Ae^{2t} + 6Ae^{2t} = 6e^{2t}$$

$$20A = 6$$

$$A = \frac{3}{10}$$

$$y(t) = \frac{3}{10}e^{2t}$$

Finally, $y'' + 5y' + 6y = 6\frac{1}{3} \cos t$. There are several ways to solve this equation, such as Method of Undetermined Coefficients, Phasors, and also a strategy that involves converting the cosine to exponentials. The route taken in class was to convert to exponentials. So...

$$y'' + 5y' + 6y = 6\frac{1}{3} \cos t = \frac{1}{2}(e^{-jt} + e^{jt})$$

We now generalize the approach. Suppose $H(s^2 + 5s + 6)e^{st} = 6e^{st}$.

$$H(s) = \frac{6}{s^2 + 5s + 6}$$

Input	S.S. Output
e^{st}	$H(s)e^{st}$
$\frac{1}{2}e^{jt}$	$\frac{1}{2}H(s)e^{jt}$
$\frac{1}{2}e^{-jt}$	$\frac{1}{2}H(s)e^{-jt}$

$H(s)$ is called the *transfer function*.

$$\frac{3}{5(1+j)} = \frac{3}{5\sqrt{2}}e^{-j\frac{\pi}{4}}e^{jt} + \frac{3}{5\sqrt{2}}e^{j\frac{\pi}{4}}e^{-jt}$$

$$\begin{aligned} y_p(t) &= \frac{3}{5\sqrt{2}}(2) \cos\left(t - \frac{\pi}{4}\right) \\ &= \frac{6}{5\sqrt{2}} \left[\frac{\sqrt{2}}{2} \cos t + \frac{\sqrt{2}}{2} \sin t \right] \end{aligned}$$

That concludes notes from “the most important lecture of (my) life.” >_>

3 Filters (Lecture 3)

There are several types of filters.

- Low-pass filter - passes low-frequency signals and attenuates signals with frequencies higher than the cutoff frequency
- High-pass filter - passes high-frequency signals and attenuates signals with frequencies lower than the cutoff frequency
- Band-pass filter - passes signals with frequencies in a certain range and attenuates other signals with frequencies outside that range (a combination low- and high-pass filter)
- Band-stop (or band-rejection) filter - attenuates signals with signals within a certain range

4 Amplification (Lecture 3)

Frankly, the prof's first lecture on amps (lecture 3) was utter crap, but here's some random data. It's probably fits better in a section on complex analysis.

$$H(s) = \frac{6}{s^2 + 5s + 6}$$

ω	$ H(j\omega) $	$\angle H(j\omega)$	$H(j\omega)$
0	1	0	?
1	$\frac{6}{\sqrt{50}}$	$-\frac{\pi}{4}$	$\frac{6}{5+5j}$
3	$\frac{6}{\approx 15}$	$-\arctan \frac{15}{-3} + \frac{\pi}{4}$	$\frac{6}{-3+15j}$
∞	0	$-\pi$	-

5 Transfer Function & Frequency Response (Lecture 4)

Math dump (for some circuit not pictured here yet). Also, wiki.

$$V_L + V_R + V_C = y$$

$$i = C \frac{dy}{dt} \quad V_L = L \frac{di}{dt} = LCy''(t)$$

$$V_R = Ri = RCy'(t) + y(t) = x$$

$$y''(t) + \frac{R}{L}y'(t) + \frac{1}{LC}y(t) = \frac{1}{RC}x$$

$$x(t) = e^{st}, \quad y_p(t) = H(s)e^{st}$$

$$H \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right) e^{st} = \frac{1}{LC}e^{st}$$

$$H(s) = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

s_1 and s_2 are the roots of the transients and occur in some sort of $e^{s_1 t} / e^{s_2 t}$ factors.

To find the frequency response, look at e^{st} .

Poles The roots of the denominator are called the *poles*, and have the form $s = -\frac{R}{2L} \pm$ some complex part. If the roots are in the left of the complex plane (negative real part), the system is *stable*.

5.1 Graphically Computing Gain and Phase

Consider the following transfer function.

$$H(s) = \frac{6}{s^2 + 5s + 6} = \frac{6}{(s + 2)(s + 3)}$$

Draw $H(j\omega)$ on the complex plane (not pictured yet). No wait, screw that.

$$|H(j\omega)| = \frac{6}{ab}$$

$$\angle H(j\omega) = 0 - (\alpha + \beta)$$

Suppose $\omega = 0$ (DC gain).

$$\text{gain} = \frac{6}{(-2)(-3)} = 1$$

$$\text{phase} = 0 - (0 + 0) = 0$$

Suppose $\omega = 2$.

$$\text{gain} = \frac{6}{\sqrt{8}\sqrt{13}}$$

6 Pointless Shit (Lecture ALL)

6.1 All Electrical Engineers are Also Mechanical Engineers

Because if you can analyze a linear circuit, a 10000 kg mass is just the same thing.

RLC Circuit	10000 kg Mass
v	f
$p = vi$	$p = fv$
$R = \frac{v}{i}$	$B = \frac{f}{v}$
$v = L \frac{di}{dt}$	$f = M \frac{dv}{dt}$
$v = \frac{1}{C} \int i dt$	$f = Kx$

