
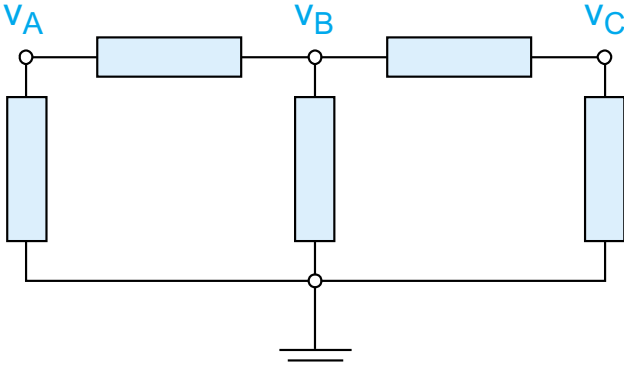


Node voltages:

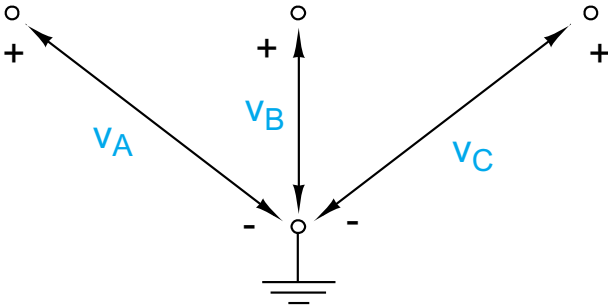

Notation




Interpretation


If the K th two-terminal element is connected between nodes X and Y , then the element voltage can be expressed in terms of the two node voltages as

$$V_k = V_x - V_y$$

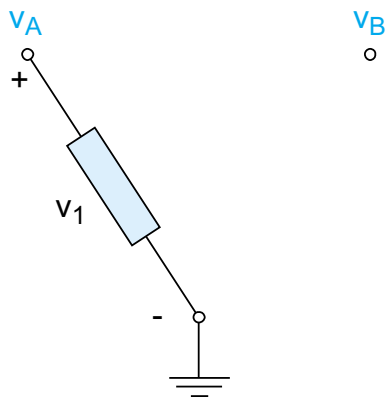where X is the node connected to the positive reference for element voltage v_k



Case A

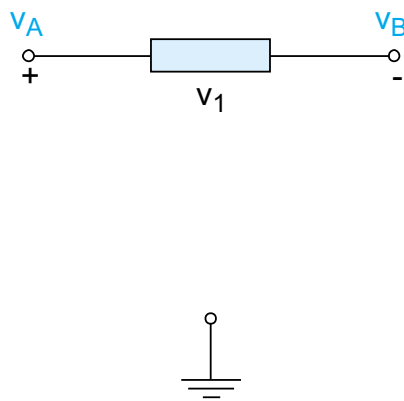


Case B

Node Voltage Method

- 1) select a reference node for ground, assign a node voltage to all other nodes and a current through every element.
- 2) write node equations via KCL
- 3) element equations (using conductance)
- 4) combine steps 2 & 3 to eliminate (non-source) element currents. In the process, reorder node equations to put all dependent values on LHS and independent values on RHS
- 5) solve for node voltages using linear algebra (you should know how to do this, see appendix B for a refresher)

Did somebody say example?

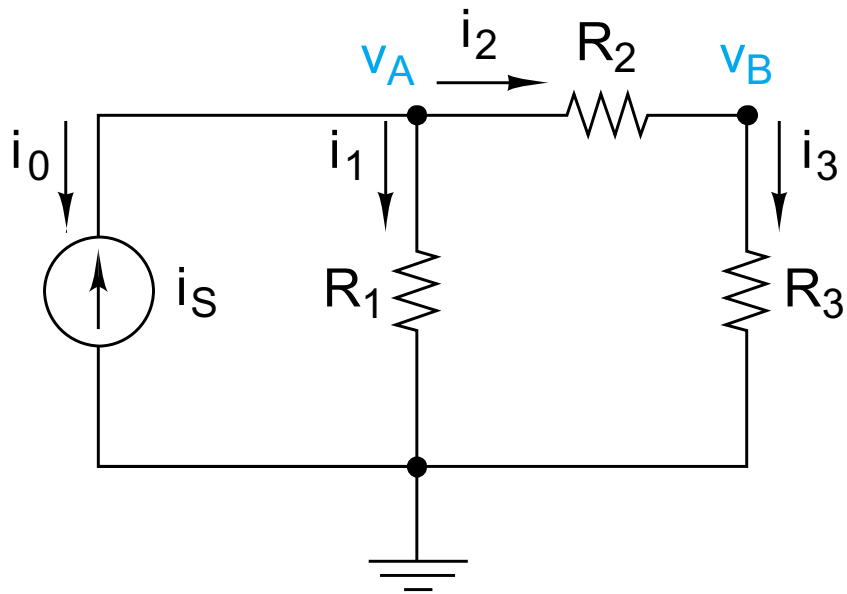


Making things quicker...

Replace steps 2-4 with modified step 2:

$$v_X \cdot (\text{sum of all conductances entering node } X) - \sum (\text{conductance } i \text{ entering node } X) \cdot v_i + \text{other currents} = 0$$

where v_i is the node voltage on the opposite side of the i -th resistor entering node X

Oh what I'd give for an example...

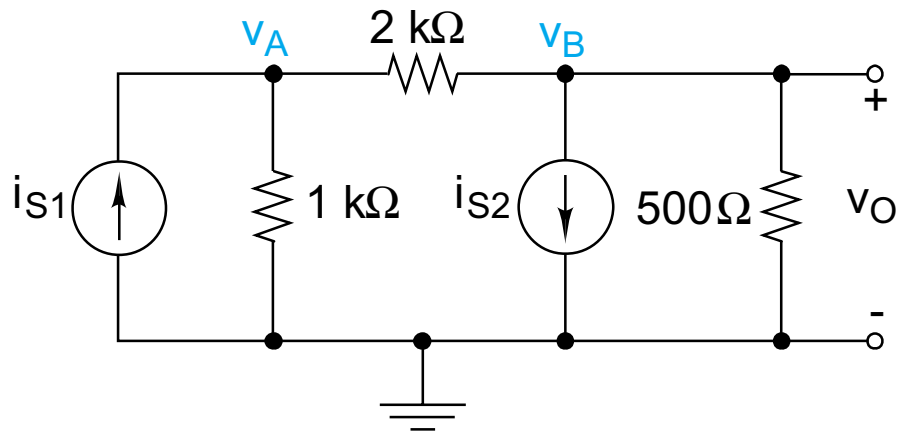

But what about voltage sources?

method 1: convert to current source


method 2: set ground at one end of voltage source. Now

$$V_A \equiv V_S$$



may not be able to do this for all voltage sources in a circuit

method 3: Super node: apply KCL to region and note that


$$V_A - V_B = V_S$$

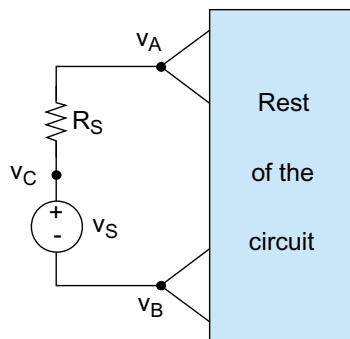

Method 1

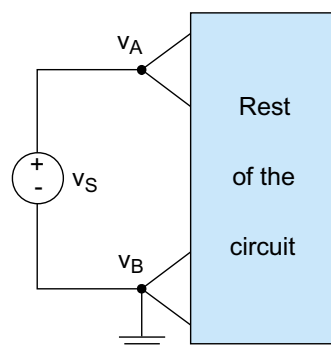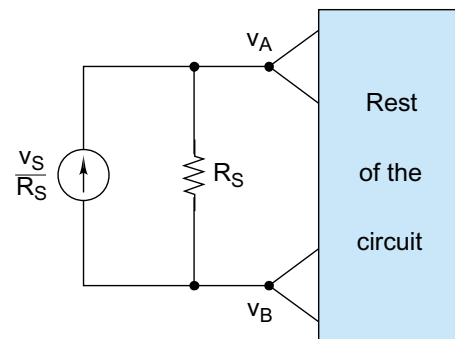

Method 2

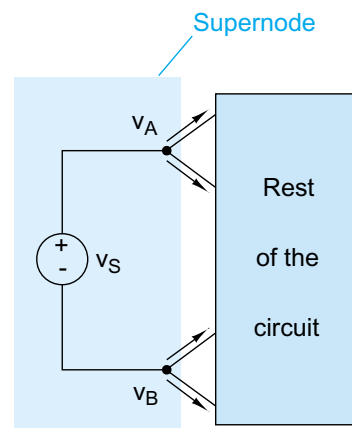

Method 3

