
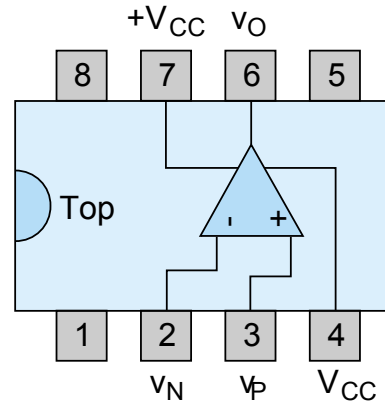



Homework set #5, due 4/30/08

4-2, 4-7, 4-13, 4-14, 4-16, 4-17, 4-20, 4-21, 4-23, 4-26

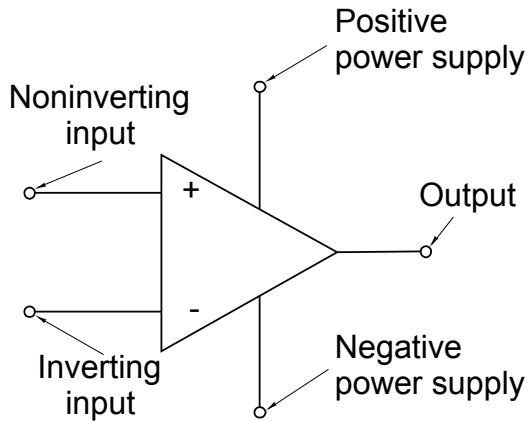
Meet the Operational Amplifier, its friends call it "the Op Amp"



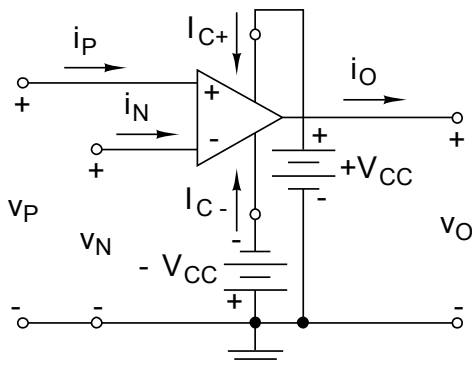This is a real device that you can buy... made up of lots of transistors and stuff. We will be working with a few simple models of the Op Amp...




$$i_O = I_{C+} + I_{C-} + i_P + i_N$$

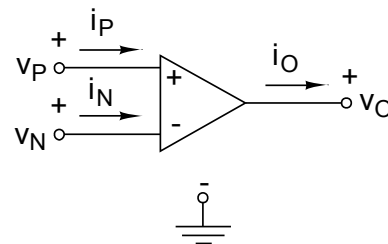

$$i_O \neq i_P + i_N$$

Transfer characteristic for an Op Amp

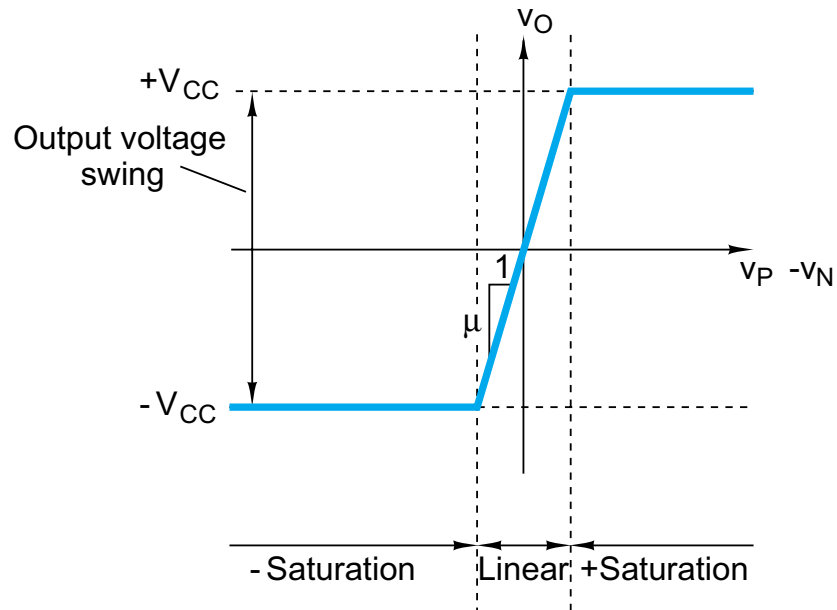


noninverting input	V_P
inverting input	V_N
output voltage	V_O
voltage gain	μ

$$V_O = \mu(V_P - V_N)$$

3 modes of operation:

- saturation
- linear
- + saturation

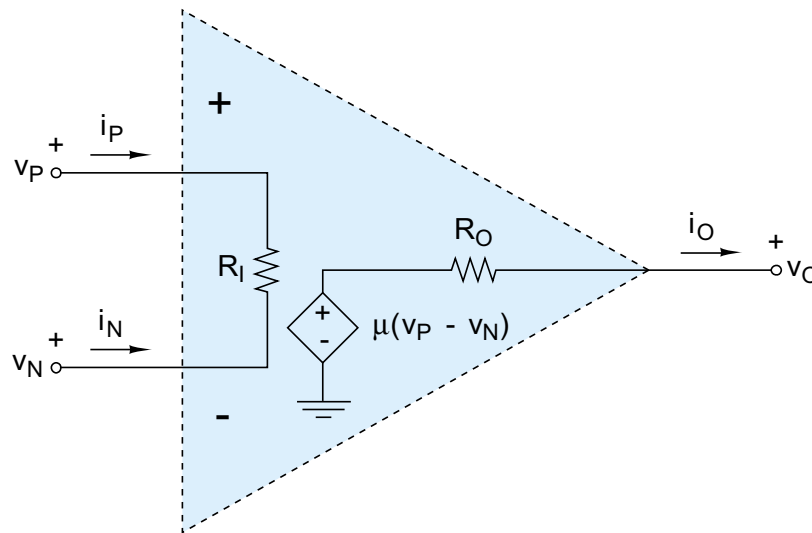Model of an Ideal Op Amp operating in the linear region



$$R_1 \in [10^6, 10^{12}] \Omega$$

$$R_O \in [10, 100] \Omega$$

$$\mu \in [10^5, 10^8]$$

$$-V_{CC} < v_O < +V_{CC}$$

$$-V_{CC}/\mu < (v_P - v_N) < +V_{CC}/\mu$$


Since $V_{CC} \sim 15V$; $\mu \gg 0$, $(v_P - v_N) \approx 0$

Next, we assume $\mu \rightarrow \infty$ and arrive at the "ideal model" of the Op Amp:

$$v_P = v_N$$

$$i_P = i_N = 0$$


In other words (pictures?)

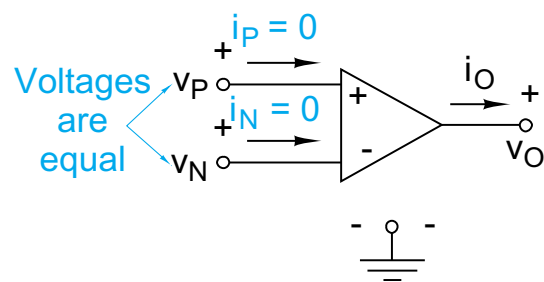

Now for the final piece of the puzzle: feedback.


Feedback ensures $(v_P - v_N) \approx 0$ and thus, keeps the Op Amp in the linear region.

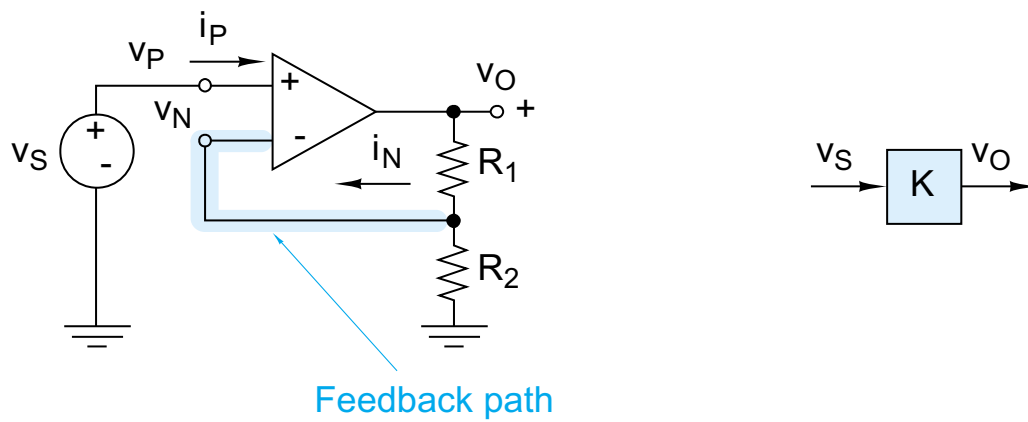My friends call me an example- I'm a non-inverting Op Amp circuit




K = closed loop gain (of the circuit)

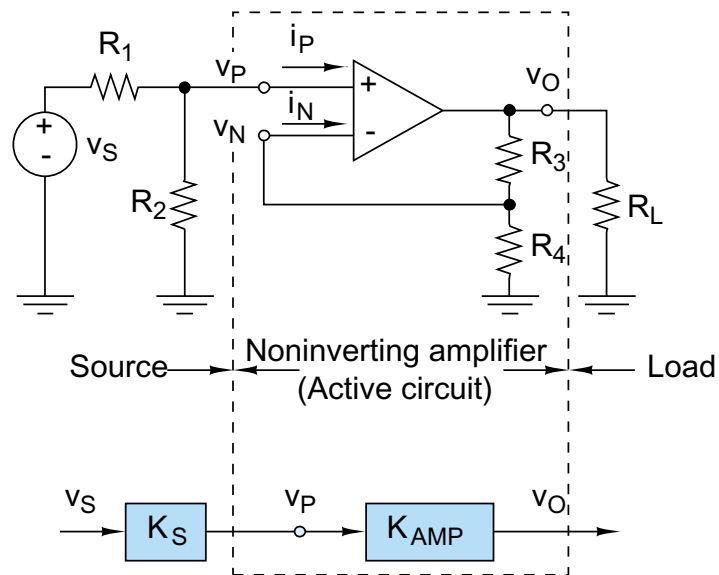Placing the non-inverting Op Amp circuit into a larger circuit...



Now for a voltage follower

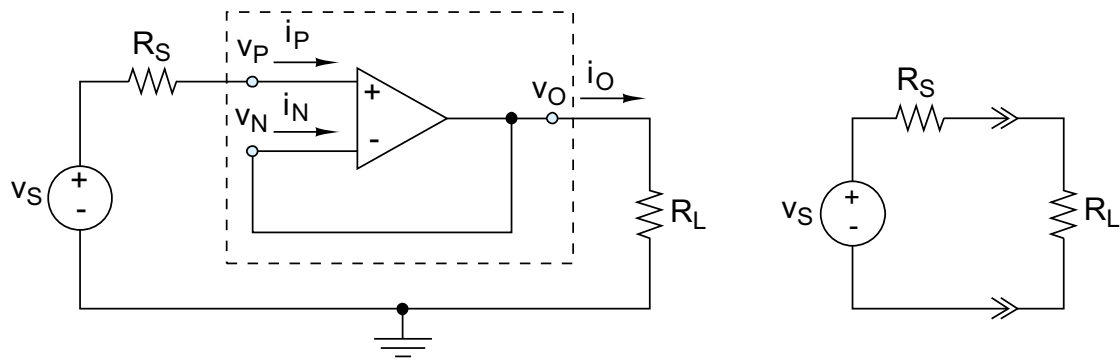

And an inverting amplifier

