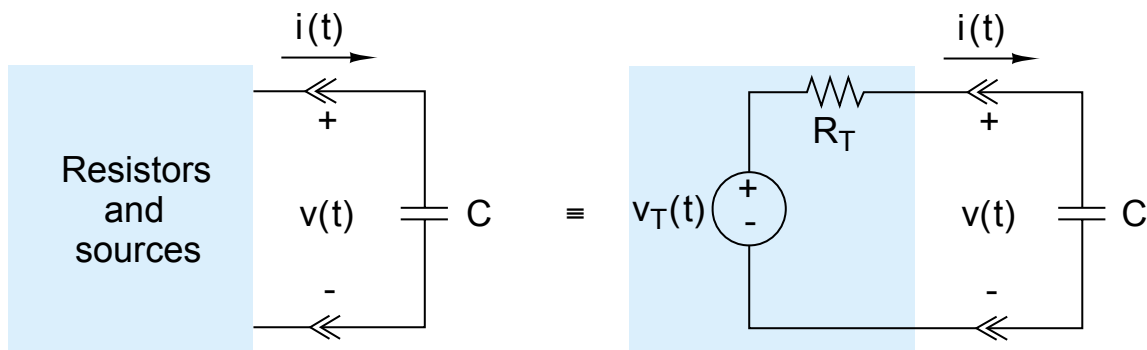


Homework set #7, due 5/14/08

6-2, 6-6, 6-10, 6-24, 6-40, 7-7, 7-13, 7-14, 7-23, 7-26, 7-28

First Order circuits- RC & RL

RC - can you reduce the given circuit to a single resistor and a single capacitor?



Capacitor constraint:

$$i(t) = C \frac{dv(t)}{dt}$$

Choose an equivalent circuit with independent variable $i(t)$ for everything else => Thevenin


$$R_T i(t) + v(t) = v_T(t)$$

Combining constraints:

$$R_T C \frac{dv(t)}{dt} + v(t) = v_T(t)$$

Other things to touch on: the state variable, the fact that it is a 1st order LDE w/ constant coefficients, what's the input and output

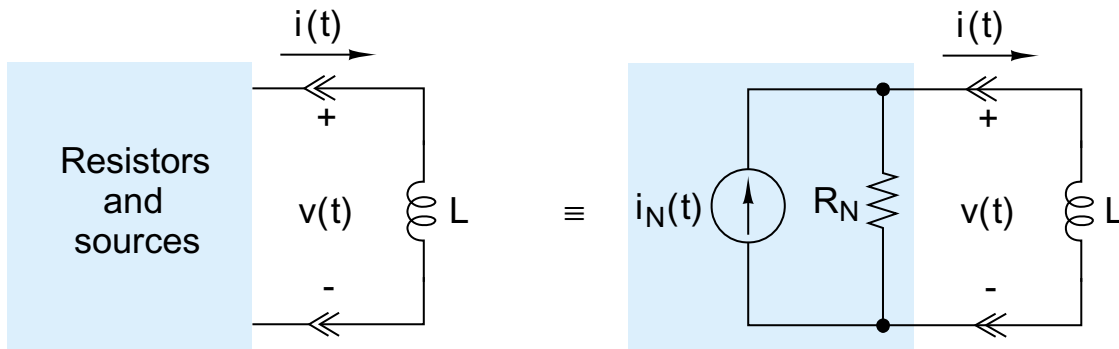RL - can you reduce the given circuit to a single resistor and a single inductor?



Inductor constraint:

$$v(t) = L \frac{di(t)}{dt}$$

Choose an equivalent circuit with independent variable $v(t)$ for everything else \Rightarrow Norton

$$G_N v(t) + i(t) = i_N(t)$$

Combining constraints:

$$G_N L \frac{di(t)}{dt} + i(t) = i_N(t)$$

Other things to touch on: the state variable, the fact that it is a 1st order LDE w/ constant coefficients, what's the input and output

Duality...

How do you solve these beasts? Three factors contribute to our solution:

- 1) The input(s) driving the circuit (e.g., $v_T(t)$)
- 2) The values of the circuit parameters (e.g., R_T and C)
- 3) The initial stored energy (initial condition) (e.g., $v(0)$)


(1) and (2) apply to any linear circuit, but (3) is new

To address (3) we must find the "zero-input" or "natural" response

$$R_T C \frac{dv(t)}{dt} + v(t) = 0$$

This is a homogeneous equation, so $v(t)$ and its derivative must have the same form. Only one family of functions satisfy this condition:


$$v(t) = Ke^{st}$$

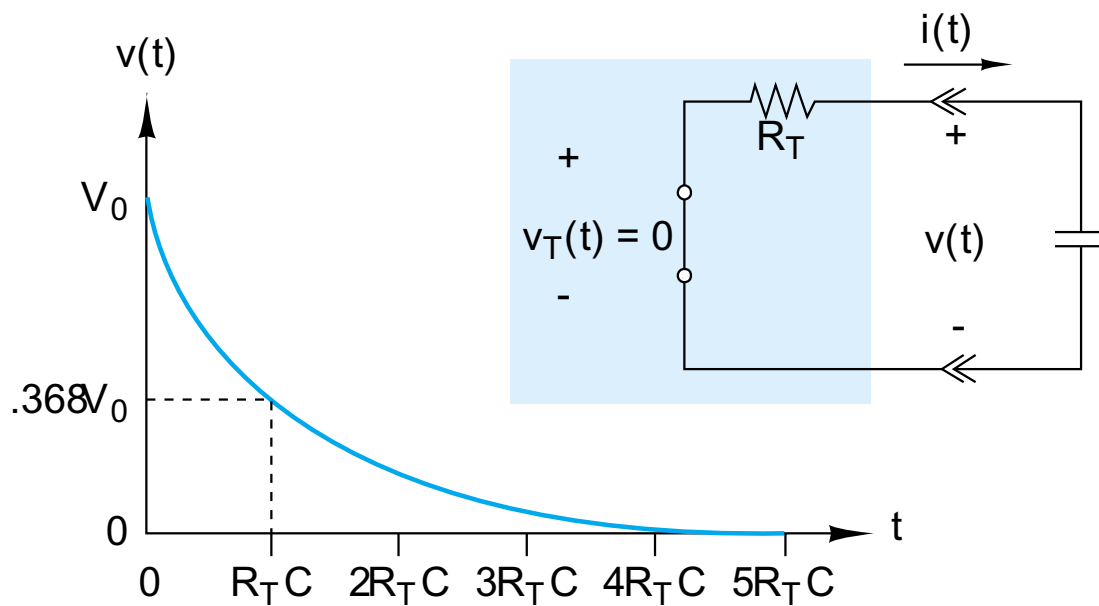


$$v(t) = V_0 e^{-t/R_T C}, \quad t \geq 0$$

Can you identify the characteristic equation and time constant? What about repeating the exercise for the RL circuit?


Try this on for size

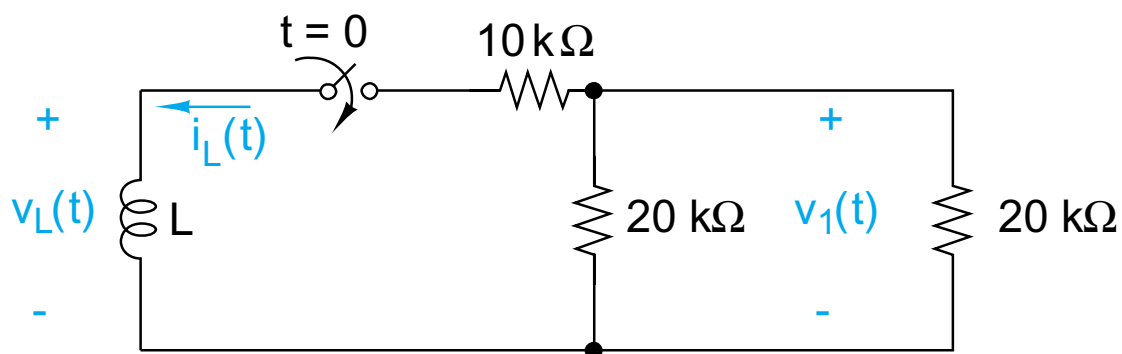

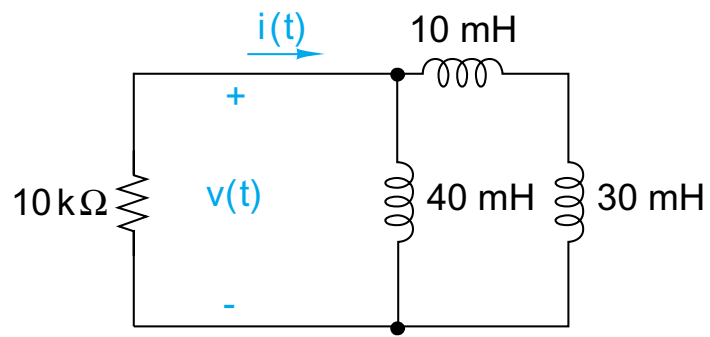Given $L=40\text{mH}$ and $I_0=-50\text{mA}$, solve for $v_L(t)$ and $v_1(t)$



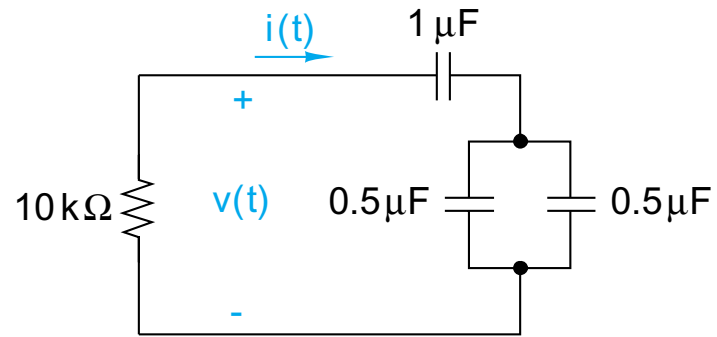Given $I_0 = 100\text{ mA}$, solve for $v(t)$



Given $V_O=3\text{V}$, solve for $i(t)$

But what if I can't find the equivalent circuit???

